
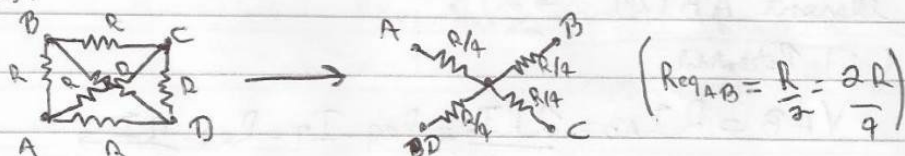


2. We gonna approach this problem by making an equivalent circuit; we can express a corner graph by a Y circuit (if all resistances are equal):

Examples:

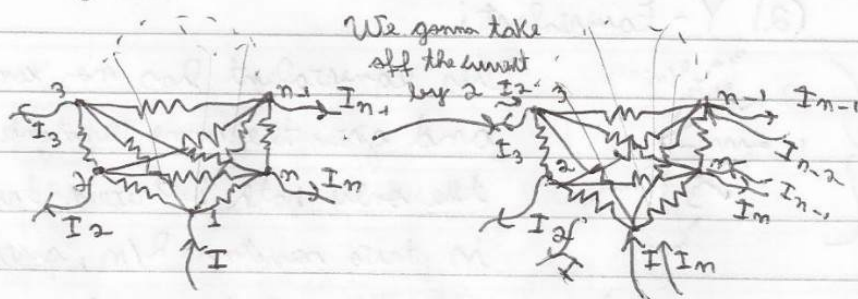

In general, the equivalent resistance between two points in this kind of graph is $2R/n$, being n the number of vertices; we can prove this by using that; if we put a current I in one vertex, we gonna have something like:



Now in a system in we pull a current I from a node and take by the other, we don't have current entering the others, so:


$$I_2 = I_3 = I_4 = \dots = I_n$$

$$\rightarrow \text{if } I = I_2 + I_3 + I_4 + \dots + I_n = (n-1)I_2 \rightarrow$$

$$\rightarrow \boxed{I_2 = \frac{I}{n-1}}$$

$\rightarrow$ the current flowing out of any node is $I/(n-1)$ and

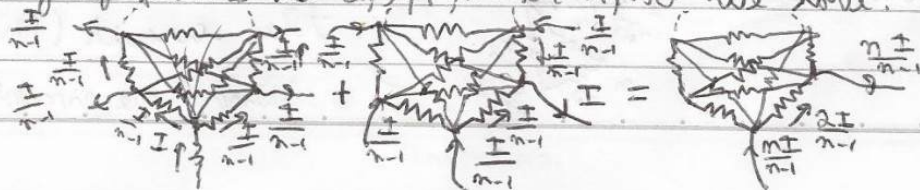Now & we have symmetry this works too for the current going from 1 to 2, 3, 4, ..., or n , so we have:



So, using superposition we have a circuit with current only entering A and just leaving B, and is easy to find the potential difference AB in function of I, because we know the element AB (at $1 \rightarrow 2$):


(1) Potential

$$V_{AB} = R I_{AB} = \frac{2RI}{n-1} = R_{eq} \cdot I \Rightarrow R_{eq} = \frac{nI}{n-1}$$

$$\Rightarrow \boxed{R_{eq} = \frac{2R}{n}}$$

And, for symmetry, this is the same resistance for any two vertex, so we can represent this circuit by:


(2) Y-Equivalent:

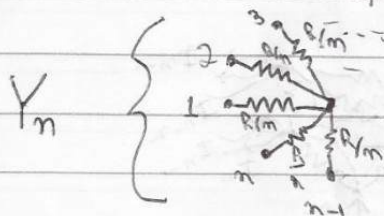

This equivalent has no connections and gives the same resistance, because the only path between two vertex is two resistors R/n , giving the


same response, there's no difference between the systems.

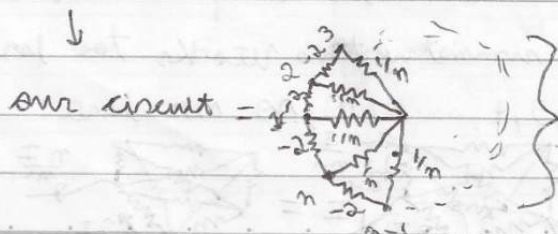Now, the key idea is to transform our circuit that is a complex thing, into a "small" circuit. We can see our circuit as a superposition of two ones:




So, we gonna solve this circuit (that is way more simple).

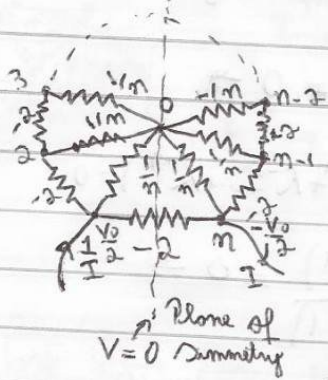We gonna set with a battery the diff between the node 1 and n , being the $1 = V_0/2$ and $n = -V_0/2$, so:



In the node between all others (the center 0) the potential is zero, by the symmetry of the system, so we can easily find the current between a node and "0", so we gonna look to a node "k".

(3) Continuity of current:

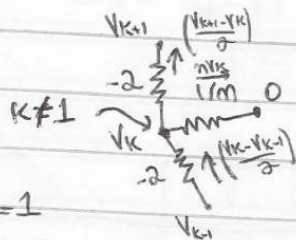

in $k=1$
we have a
source of current,
so the equation
is not valid.

$$\underbrace{\frac{V_{k+1} - V_k}{2}}_{\text{current getting out of } k} + \underbrace{n V_k}_{\text{current entering } k} = \underbrace{\frac{V_k - V_{k-1}}{2}}_{\text{current entering } k}$$

$$V_{k+1} + 2(n-1)V_k + V_{k-1} = 0$$

This is a second-order linear recurrence, with solutions of the form $V_k \sim \lambda^k \rightarrow$

$$\rightarrow \lambda^{k+1} + 2(n-1)\lambda^k + \lambda^{k-1} = 0 \rightarrow$$

$$\rightarrow \lambda^2 + 2(n-1)\lambda + 1 = 0 \rightarrow$$

$$\rightarrow \lambda_{\pm} = \frac{-2(n-1) \pm \sqrt{4(n-1)^2 - 4}}{2}$$

Let us define $\lambda_+ = \lambda = \frac{-2(n-1) + \sqrt{4(n-1)^2 - 4}}{2}$, and by $\lambda_+ \lambda_- = 1 \rightarrow \lambda_- = 1/\lambda$, how $\lambda_{\pm}$ is solution, a linear combination of those also is, so:

$$V_k = a \lambda^k + b \lambda^{-k}$$

And, using that $\frac{dQ}{dt}$ in 0 we can't have charge varying in time, the net current is zero:

$$\sum_{k=1}^{K=n} I_k = \sum_{k=1}^{K=n} (a\lambda^k + b\lambda^{-k}) = 0 \rightarrow$$

$$\rightarrow a(\lambda + \lambda^2 + \dots + \lambda^n) + b(\lambda^{-1} + \lambda^{-2} + \dots + \lambda^{-n}) = 0$$

$$\rightarrow a\lambda \frac{(\lambda^n - 1)}{\lambda - 1} + b \frac{(\frac{1}{\lambda^n} - 1)}{\frac{1}{\lambda} - 1} = 0 \rightarrow$$

$$\rightarrow a\lambda \frac{(\lambda^n - 1)}{\lambda - 1} + \frac{b}{\lambda^{n+1}} \left(\frac{\lambda^n - 1}{\lambda - 1} \right) = 0 \xrightarrow{\text{being } \lambda \neq 1}$$

$$\rightarrow \boxed{b = -a\lambda^{n+1}}$$

Which implies that:

$$\boxed{V_k = a(\lambda^k - \lambda^{n+1-k})} \rightarrow V_k = V_{n-k} \text{ and if } k = \frac{n+1}{2} \Rightarrow V = 0 \text{ (plane of symmetry)}$$


$$\text{Using that } V_1 = \frac{V_0}{2} \rightarrow$$

$$\rightarrow V_1 = a(\lambda - \lambda^n) = \frac{V_0}{2} \rightarrow \boxed{a = \frac{V_0}{2\lambda(1 - \lambda^{n-1})}}$$


$$\rightarrow \boxed{V_k = \frac{V_0}{2\lambda(1 - \lambda^{n-1})} (\lambda^k - \lambda^{n+1-k})}$$

We can now find the relationship between V_0 and I , that is the net current entering and leaving the system, and with this we find the resistance!
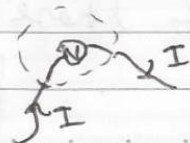
$$\boxed{R_{eq} = \frac{\Delta V}{I_0} = \frac{V_0}{2} - \left(-\frac{V_0}{2} \right) = \frac{V_0}{I_0}}$$



Using OHM's LAW and Kirchhoff's

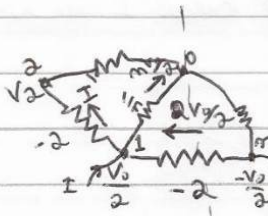

$$I' = I_2 = I - \left(\frac{n}{2} - \frac{1}{2}\right) V_0 \rightarrow$$

$$\rightarrow V_2 - V_1 = -(-2)I' = 2I - (2\frac{n}{2} - 1)V_0 =$$

$$\Delta V = 2I - (n-1)V_0$$

And, by our formula:

$$\begin{aligned} \Delta V = V_2 - V_1 &= a(k^2 - k^{n-1}) - a(k' - k^n) = \\ &= a[k(k-1) + k^{n-2}(k-1)] = \\ &= a k (k-1)(1 + k^{n-2}) \end{aligned}$$

$$\Delta V = \frac{V_0 (k-1)(1 + k^{n-2})}{2(1 - k^{n-1})}$$

$$\rightarrow 2I - (n-1)V_0 = \frac{V_0 (k-1)(1 + k^{n-2})}{2(1 - k^{n-1})} \rightarrow$$

$$\rightarrow R_{eq} = \frac{V_0}{I} = \frac{2}{n-1 + \frac{(k-1)(1 + k^{n-2})}{2(1 - k^{n-1})}} \quad \text{Ohm's}$$

being $k = -(n-1) + \sqrt{(n-1)^2 - 1}$, and n a integer representing the number of nodes, and:

$$\begin{aligned} R_3 &= R_{eq_3} = \frac{4}{3} \Omega \\ R_4 &= R_{eq_4} = \frac{5}{6} \Omega \\ R_5 &= R_{eq_5} = \frac{32}{55} \Omega \end{aligned}$$