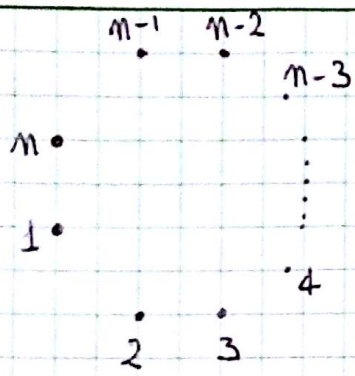




We have n vertices

Let V_i be the potential on the i -vertex

Let $V_1 = -1/2 V$ and $V_n = 1/2 V$

Let I_{ij} be the direct current from i to j

(it does not flow in any vertex different from either i or j).

As clear from the sketch, we have a vertical symmetry, so that $V_1 = -V_n$, $V_2 = -V_{n-1}$, ..., $V_i = -V_{n-i+1}$

As a consequence:

$$\sum_{i=1}^n V_i = 0V \quad (1)$$

Let's find all the I_{ij} values for a generic $i \neq 1, n$. Their sum must be equal to 0A due to Kirchhoff's law.

$$I_{i,i-1} = (V_i - V_{i-1}) \cdot \frac{1}{2\Omega}$$

$$I_{i,i+1} = (V_i - V_{i+1}) \cdot \frac{1}{2\Omega}$$

In all the other cases we have that

$$I_{i,j} = (V_i - V_j) \cdot \frac{1}{1\Omega} \quad \forall j \neq i-1, i+1$$

Note that there is no problem in including also $j = i$ (and, indeed, we are doing so)

We may now consider and evaluate the summation of the different $I_{i,j}$ for a fixed i , keeping in mind Kirchhoff's law:

$$\begin{aligned} \sum_{j=1}^n I_{ij} &= I_{i,1} + I_{i,2} + \dots + I_{i,n} = I_{i,1} + \dots + I_{i,i-1} + I_{i,i} + \\ &+ I_{i,i+1} + \dots + I_{i,n} = \frac{(V_i - V_1)}{1\Omega} + \dots + \frac{(V_i - V_{i-1})}{2\Omega} + \\ &+ \frac{(V_i - V_i)}{1\Omega} + \frac{(V_i - V_{i+1})}{2\Omega} + \dots + \frac{(V_i - V_n)}{1\Omega} = 0 \text{ A} \Rightarrow \end{aligned}$$

$$\Rightarrow (n-1)V_i - \sum_{j=1}^n V_j + \frac{V_{i-1}}{2} + \frac{V_{i+1}}{2} = 0 \text{ V}$$

This result is true for each generic vertex i which is not connected (directly) with an external circuit. So it is true if $2 \leq i \leq n-1$. ~~Using~~ Using equivalence (1):

$$2(n-1)V_i + V_{i+1} + V_{i-1} = 0 \text{ V}$$

$$\Rightarrow V_{i+1} + 2(n-1)V_i + V_{i-1} = 0 \text{ V}$$

Now we should turn this recursive property into an explicit form (it's "just" math):

$$x^2 + 2(n-1)x + 1 = 0 \Rightarrow x_{1,2} = 1-n \pm \sqrt{n^2 - 2n}$$

~~8~~

$$\lambda_+ = 1-n + \sqrt{n^2 - 2n}$$

$$\lambda_- = 1-n - \sqrt{n^2 - 2n}$$

$$V_i = a \lambda_+^i + b \lambda_-^i$$

$$V_1 = a \lambda_+ + b \lambda_- = -\frac{1}{2} V \Rightarrow b = \frac{-\frac{1}{2} V - a \lambda_+}{\lambda_-}$$

$$V_n = a \lambda_+^n + b \lambda_-^n = \frac{1}{2} V \Rightarrow a = \frac{1}{2} V \cdot \frac{\lambda_-}{\lambda_+^n - \lambda_+ \cdot \lambda_-^{n-1}}$$

$$b = \frac{1}{2} V \cdot \frac{1 + \lambda_+^{n-1}}{\lambda_-^n - \lambda_- \cdot \lambda_+^{n-1}}$$

$$\Rightarrow V_i = \frac{1}{2} V \cdot \left[\lambda_+^i \cdot \frac{1 + \lambda_-^{n-1}}{\lambda_+^n - \lambda_+ \lambda_-^{n-1}} + \lambda_-^i \cdot \frac{1 + \lambda_+^{n-1}}{\lambda_-^n - \lambda_- \lambda_+^{n-1}} \right]$$

Let's now consider the case $i=1$. The ~~entering~~ negative exiting current $I_{1,2} + I_{1,3} + \dots + I_{1,n}$ is simply the total entering current in 1, and due to Kirchhoff's law, it is the total current which flows in the circuit, which has a total ~~voltage~~ "voltage" of $V_n - V_1 = 1V$. Using Ohm's 1st law and naming R_{TOT} the total resistance of the circuit:

$$R_{TOT} = \frac{1V}{-\sum_{j=1}^n I_{1,j}}$$

$$\begin{aligned} \sum_{j=1}^n I_{1,j} &= \left[\frac{V_1 - V_2}{2} + (V_1 - V_3) + \dots + (V_1 - V_{n-1}) + \frac{V_1 - V_n}{2} \right] \Omega^{-1} = \\ &= \left[(n-1)V_1 - \sum_{j=1}^n V_j + \frac{V_2}{2} + \frac{V_n}{2} \right] \Omega^{-1} \end{aligned}$$

So we need V_2 :

$$\begin{aligned}
 V_2 &= \frac{1}{2} V \cdot \left[\lambda_+^2 \cdot \frac{1 + \lambda_-^{n-1}}{\lambda_+^n - \lambda_+ \lambda_-^{n-1}} + \lambda_-^2 \cdot \frac{1 + \lambda_+^{n-1}}{\lambda_-^n - \lambda_- \lambda_+^{n-1}} \right] = \\
 &= \frac{1}{2 (\lambda_+^{n-1} - \lambda_-^{n-1})} \left[\lambda_+ (\lambda_-^{n-1} + 1) - \lambda_- (\lambda_+^{n-1} + 1) \right] V \\
 &= t V \quad \text{where } t = \frac{\lambda_+ (\lambda_-^{n-1} + 1) - \lambda_- (\lambda_+^{n-1} + 1)}{2 (\lambda_+^{n-1} - \lambda_-^{n-1})} \text{ is a pure number}
 \end{aligned}$$

Then:

$$\begin{aligned}
 \sum_{j=1}^n \bar{I}_{1,j} &= \left[(n-1) \cancel{V_1} + \frac{V_2}{2} + \frac{V_n}{2} \right] \Omega^{-1} = \\
 &= \left[(n-1) \left(-\frac{1}{2}\right) + \frac{t}{2} + \frac{1}{4} \right] A = \left[-\frac{1}{2}n + \frac{3}{4} + \frac{t}{2} \right] A \Rightarrow
 \end{aligned}$$

$$\Rightarrow R_{TOT} = \frac{1V}{\left[\frac{1}{2}n - \frac{3}{4} - \frac{t}{2} \right] A} = \frac{4 \Omega}{2n - 3 - 2t}$$

FOR $n=3$ $R_{TOT} = \frac{4}{3} \Omega$

FOR $n=4$ $\lambda_+ = -3 + 2\sqrt{2}$ $\lambda_- = -3 - 2\sqrt{2}$
 $t = 3/35$ $R_{TOT} = \frac{140}{169} \Omega$

FOR $n=5$ $\lambda_+ = -4 + \sqrt{15}$ $\lambda_- = -4 - \sqrt{15}$
 $t = 1/16$ $R_{TOT} = \frac{32}{55} \Omega$