

ELVINAS RIBINSKAS


$R_n = ?$

$R_s = 2\Omega$


$R_d = 1\Omega$

n

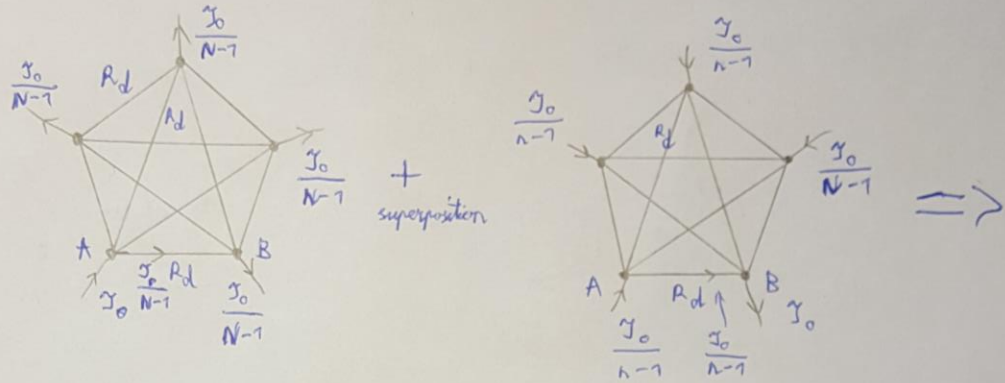[1.] Let us initially consider the same similar circuits that has all resistances equal to R_d . all the points are equivalent.



\Rightarrow

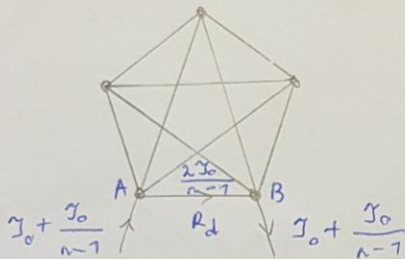

If R_{AB} is the resistance between points A and B, then


$$\frac{2\gamma_0}{n-1} R_d = U_{AB} = \left(\gamma_0 + \frac{\gamma_c}{n-1} \right) R_{AB}$$

$$\parallel$$

$$\checkmark$$


$$R_{AB} = \frac{2 R_d}{n}$$

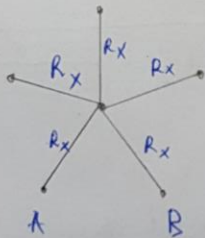Resistances between any two points are equal, hence, this circuit the equivalent circuit looks like that:



, where $R_x = R_{AB} / 2 = \frac{R_d}{n}$,




[2.] We will find resistance r such that

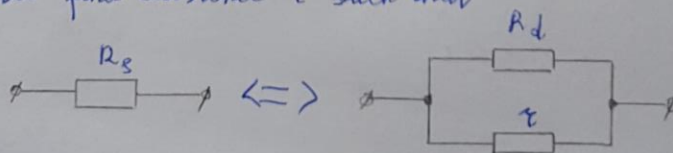

The total resistance of this circuit


$$\frac{R_d z}{R_d + z} = R_s \Rightarrow z = \frac{R_s R_d}{R_d - R_s}$$

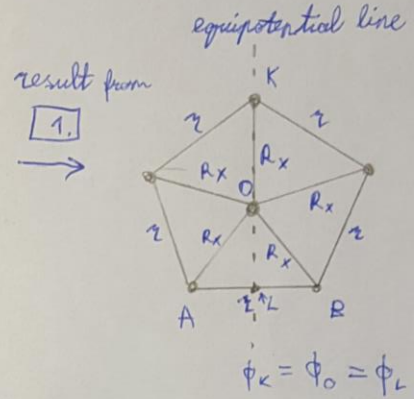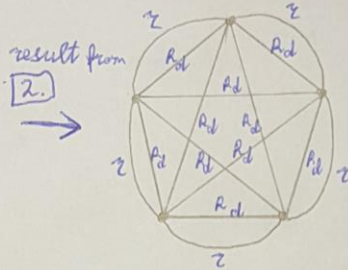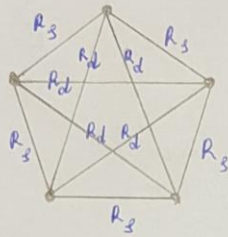3. We can use equivalencies found in 1. and 2. to simplify the circuit.



Here $R_x = \frac{R_d}{n}$ and $z = \frac{R_s R_d}{R_d - R_s}$

4. The last circuit is equivalent to

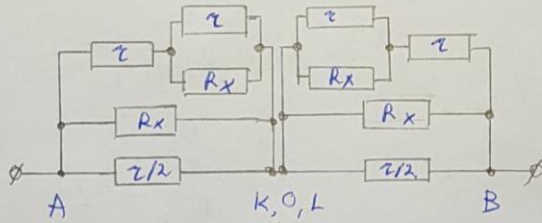

Thus, for $n=5$

$$R_5 = 2 \frac{1}{\frac{1}{z/2} + \frac{1}{R_x} + \frac{1}{z + \frac{1}{\frac{1}{z} + \frac{1}{R_x}}}}$$

Similarly, for any odd n


~~$$R_n = \frac{2}{\frac{2}{z} + \frac{1}{R_x} + \frac{1}{z + \frac{1}{\frac{1}{R_x} + \frac{1}{z + \frac{1}{\frac{1}{R_x} + \frac{1}{z + \dots}}}}}}$$~~

$$R_n = \frac{2}{\frac{2}{z} + \frac{1}{R_x} + \frac{1}{z + \frac{1}{\frac{1}{R_x} + \frac{1}{z + \frac{1}{\frac{1}{R_x} + \frac{1}{z + \dots}}}}}}$$


where $\frac{1}{R_x}$ occurs $\frac{n-1}{2}$ times and the continued fraction

ends with $\dots + \frac{1}{\frac{1}{R_x} + \frac{1}{z}}$, except $R_3 = \frac{2}{\frac{2}{z} + \frac{1}{R_x} + \frac{1}{z}}$

As an example of even n we take $n=6$.

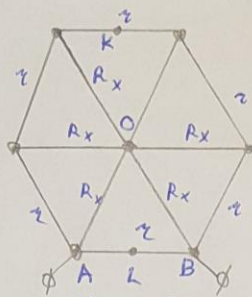

\Leftrightarrow

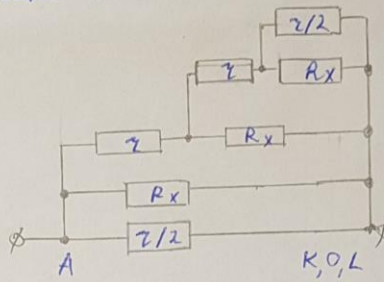

$\times 2$
(in series)

Thus, $R_6 = z \frac{1}{\frac{1}{z/2} + \frac{1}{R_x} + \frac{1}{z + \frac{1}{\frac{1}{R_x} + \frac{1}{z + \frac{1}{\frac{1}{z/2} + \frac{1}{R_x}}}}}}$

Similarly, for any even n

$R_n = \frac{2}{\frac{2}{z} + \frac{1}{R_x} + \frac{1}{z + \frac{1}{\frac{1}{R_x} + \frac{1}{z + \frac{1}{\frac{1}{R_x} + \frac{1}{z + \dots}}}}}}$, where $\frac{1}{R_x}$ occurs $\frac{n}{2}$ times

and the continued fraction ends with

$\dots + \frac{1}{\frac{1}{R_x} + \frac{2}{z}}$

5. $R_x = \frac{R_d}{n} = \frac{1 \Omega}{N}$; $z = \frac{R_s R_d}{R_d - R_s} = -2 \Omega$

$R_3 = \frac{2}{\frac{2}{z} + \frac{1}{R_x} + \frac{1}{z}} = \frac{4}{3} \Omega$

$R_4 = \frac{2}{\frac{2}{z} + \frac{1}{R_x} + \frac{1}{z + \frac{1}{\frac{1}{R_x} + \frac{2}{z}}}} = \frac{5}{6} \Omega$; $R_5 = \frac{2}{\frac{2}{z} + \frac{1}{R_x} + \frac{1}{z + \frac{1}{\frac{1}{R_x} + \frac{1}{z}}}} = \frac{32}{55} \Omega$