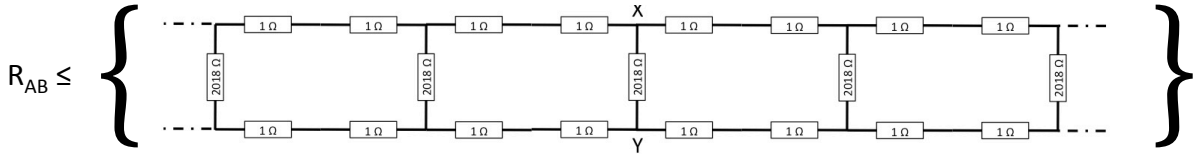
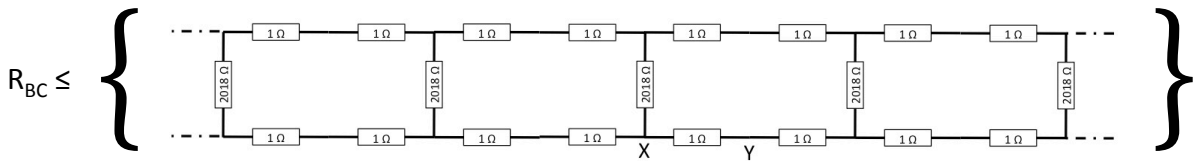




Given any resistor circuit, the removal of any nodes or connections will certainly **not decrease** the effective resistance between any pair of points. By removing all nodes and resistor connections from the infinite lattice apart from the horizontal ladder rung containing points A, B and C, we may thus **find upper bounds for  $R_{AB}$  and  $R_{BC}$** :



$$\begin{aligned} \text{Thus } R_{AB} &\leq 2018 // r // r \\ &= 2018r \div (r + 4036) \\ &= \mathbf{2018 \div \sqrt{2019}}. \quad \leftarrow \text{sub. } r = 2 + 2\sqrt{2019} \end{aligned}$$



$$\begin{aligned} \text{Thus } R_{BC} &\leq 1 // [(2018 // r) + (r - 1)] \\ &= (r^2 + 4035r - 2018) \div (r^2 + 4036r). \end{aligned}$$

An upper bound for  $R_{BC}$  gives a lower bound for  $R_{AB}$ :

$$\begin{aligned} R_{AB} = 4036 (1 - R_{BC}) &\geq 4036 [1 - (r^2 + 4035r - 2018) \div (r^2 + 4036r)] \\ &= 4036 (r + 2018) \div (r^2 + 4036r) \\ &= \mathbf{1009 \div \sqrt{2019}}. \quad \leftarrow \text{sub. } r = 2 + 2\sqrt{2019} \end{aligned}$$

Thus:  $\mathbf{1009 \div \sqrt{2019} \Omega \leq \rho = R_{AB} \leq 2018 \div \sqrt{2019} \Omega}$   
 where the upper bound is exactly twice the lower bound.