

Physics Cup Problem 1

Prathyush Poduval

January 2, 2018

We shall try to find the exact value of the resistance between the 2 points, for the general case where the 2018 Ω resistor is replaced by r

Let us choose a cartesian coordinate system with point A as the origin (thus point B is (0,-1) and the points adjacent to A are $(\pm 1, 0)$).

Assign to the point (i,j) it's potential V_{ij} and let the current being taken out of the point be I_{ij} . Writing kirchoff's node law at the point,

$$2V_{ij} - V_{i-1j} - V_{i+1j} + \frac{V_{ij} - V_{ij\pm 1}}{r} = I_{ij}$$
$$\implies V_{ij} = \frac{rI_{ij} + r(V_{i+1j} + V_{i-1j}) + V_{ij\pm 1}}{2r + 1}$$

Here, whether we choose the plus or minus in $V_{ij\pm 1}$ depends on whether $i + j$ is odd (plus) or even (minus).

Let us calculate the fourier series with the potential as coefficients (o is the root of -1)

$$F_1(x, y) = \sum_{i+j \text{ even}} V_{ij} e^{o(ix+jy)}$$
$$= \sum \frac{rI_{ij} e^{o(ix+jy)} + r(V_{i+1j} e^{o(ix+jy)} + V_{i-1j} e^{o(ix+jy)}) + V_{ij\pm 1} e^{o(ix+jy)}}{2r + 1}$$
$$= \frac{rI + \sum_{i+j \text{ odd}} V_{ij} e^{o(ix+jy)} (2r \cos(x) + e^{oy})}{2r + 1}$$

$$= \frac{rI + F_2(x, y)(2r \cos(x) + e^{oy})}{2r + 1}$$

Where we used the fact that $I_{0,-1} = I$ (current being removed) and F_2 is defined by:

$$F_2(x, y) = \sum_{i+j \text{ odd}} V_{ij} e^{o(ix+jy)}$$

Using similar line of reasoning above, we get

$$F_2 = \frac{-Ire^{-oy} + F_1(2r \cos(x) + e^{-oy})}{2r + 1}$$

Solving the 2 equations, we get

$$F_1 = \frac{Ir}{2} \frac{1 - \cos(x)e^{-oy}}{r \sin^2(x) - \cos(x) \sin(x) + 1}$$

$$F_2 = \frac{Ir}{2} \frac{\cos(x) - e^{-oy}}{r \sin^2(x) - \cos(x) \sin(x) + 1}$$

Thus we can find the resistance using $\rho = \frac{V_{00}-V_{0,-1}}{I}$, which comes out to be:

$$\rho = \frac{r}{4\pi^2} \int_{-\pi}^{\pi} \int_{-\pi}^{\pi} \frac{\cos(x) \cos(y) - 1}{r \sin^2(x) - \cos(x) \sin(x) + 1} dx dy$$

Using OCTAVE, we get $\rho = 40.436$ when $r = 2018$.

ANSWER

we can choose $r=30$ and $R=60$ and $r < \rho < R$.