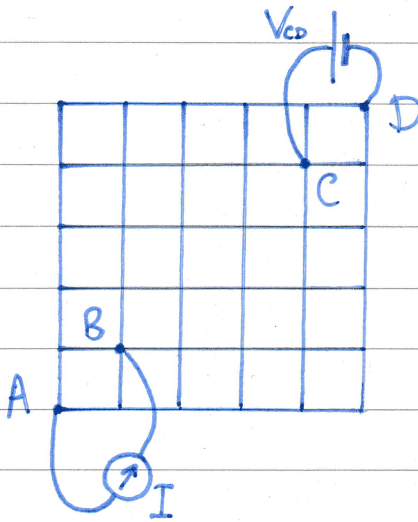


1

# Physics Cup Problem 4



Horizontal resistances:  $R$   
Vertical resistances:  $r$


Coordinates: A:  $(0, 0)$   
B:  $(1, 1)$   
C:  $(n, n)$   
D:  $(n+1, n+1)$

Before nodes C and D are shorted together, the effective resistance between nodes A and B is  $R_{11}$ . This means that if a current source producing a current  $I$  is connected between A and B, the resulting voltage between A and B will be:

$$V_B - V_A = \mathcal{E} = IR_{11}$$

In addition, nodes C and D will be raised to potentials  $V_C$  and  $V_D$  respectively. Hence, adding a battery with voltage  $V_{CD} = V_C - V_D$  between C and D as shown will not change the distribution of currents and voltages in the circuit.

What is  $V_{CD}$ ?

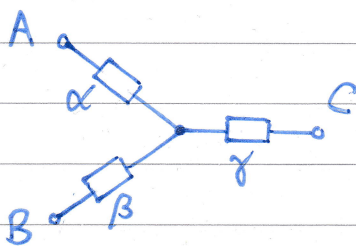

To work out  $V_C$ , we represent the circuit with terminals A, B and C as a Y-circuit as shown. We have:

$$\left. \begin{aligned} \alpha + \beta &= R_{11} \\ \alpha + \gamma &= R_{nn} \\ \beta + \gamma &= R_{n-1, n-1} \end{aligned} \right\}$$

$$\begin{aligned} \therefore \alpha &= \frac{1}{2}(R_{nn} + R_{11} - R_{n-1, n-1}) \\ \beta &= \frac{1}{2}(R_{n-1, n-1} + R_{11} - R_{nn}) \\ \gamma &= \frac{1}{2}(R_{nn} + R_{n-1, n-1} - R_{11}) \end{aligned}$$

2 If the voltages across A and B is  $\mathcal{E}$ , and if A is grounded so  $V_A = 0$ , then:

$$V_C = \mathcal{E} \left( \frac{\alpha}{\alpha + \beta} \right) \quad (\text{voltage divider formula})$$

$$= \frac{\mathcal{E}(R_{nn} + R_{11} - R_{n-1, n-1})}{2R_{11}}$$

Similarly, by replacing  $n \rightarrow n+1$  we get:

$$V_D = \frac{\mathcal{E}(R_{n+1, n+1} + R_{11} - R_{nn})}{2R_{11}}$$

$$\therefore V_C - V_D = V_{CD} = \frac{\mathcal{E}(2R_{nn} - R_{n+1, n+1} - R_{n-1, n-1})}{2R_{11}}$$

The question tells us that

$$R_{nn} = \frac{2\sqrt{R_1}}{\pi} \sum_{k=1}^n \frac{1}{2k-1} = R_{11} \sum_{k=1}^n \frac{1}{2k-1}$$

so:

$$\begin{aligned} V_{CD} &= \frac{\mathcal{E} \left[ 2R_{nn} - \left( R_{nn} + \frac{R_{11}}{2n+1} \right) - \left( R_{nn} - \frac{R_{11}}{2n-1} \right) \right]}{2R_{11}} \\ &= \frac{\mathcal{E} \left( \frac{1}{2n-1} - \frac{1}{2n+1} \right)}{2} \\ &= \frac{\mathcal{E}}{4n^2 - 1} \end{aligned}$$

Now, the superposition principle tells us that:

$$\mathcal{E} = \underbrace{\left( \text{Voltage across AB when the battery} \right)}_{= \mathcal{E}_1} + \underbrace{\left( \text{Voltage across AB when current} \right)}_{= \mathcal{E}_2}$$

(connecting C and D is shorted)      (source is made open circuit)

3 We want  $\mathcal{E}_1$ , as this will tell us the effective resistance between A and B when CD is shorted:

$$R_{11}' = \frac{\mathcal{E}_1}{I} = \frac{\mathcal{E} - \mathcal{E}_2}{I} = R_{11} - \frac{\mathcal{E}_2}{I} \quad \Rightarrow \quad R_{11}' - R_{11} = -\frac{\mathcal{E}_2}{I}$$

To get  $\mathcal{E}_2$ , we use a symmetry argument; when a voltage of  $\mathcal{E}$  is applied across AB, a potential difference of  $\frac{\mathcal{E}}{4n^2-1}$  is created between C and D. Hence, by symmetry, when a voltage of  $V_{CD}$  is applied across CD, a potential difference of  $\frac{V_{CD}}{4n^2-1}$  is created between A and B. So:

$$\mathcal{E}_2 = \frac{V_{CD}}{4n^2-1} = \frac{\mathcal{E}}{(4n^2-1)^2} \quad \Rightarrow \quad R_{11}' - R_{11} = -\frac{R_{11}}{(4n^2-1)^2} = -\frac{2\sqrt{R_T}}{\pi(4n^2-1)^2}$$