

Lower Bounds on Circuit Complexity


A. Kulikov

Steklov Institute of Mathematics at St. Petersburg

Estonian Theory Days
02 October 2009

Boolean Circuits

 - inputs: propositional variables x_1, x_2, \dots, x_n and constants 0, 1
- gates: binary functions
- fan-out of a gate is unbounded



Random Functions are Complex

Random Functions are Complex

- Shannon counting argument: count how many different Boolean functions in n variables can be computed by circuits with t gates and compare this number with the total number 2^{2^n} of all Boolean functions.

Random Functions are Complex

- Shannon counting argument: count how many different Boolean functions in n variables can be computed by circuits with t gates and compare this number with the total number 2^{2^n} of all Boolean functions.
- The number $F(n, t)$ of circuits of size $\leq t$ with n input variables does not exceed

$$(16(t + n + 2)^2)^t .$$

Each of t gates is assigned one of 16 possible binary Boolean functions that acts on two previous nodes, and each previous node can be either a previous gate ($\leq t$ choices) or a variables or a constant ($\leq n + 2$ choices).

Random Functions are Complex

- Shannon counting argument: count how many different Boolean functions in n variables can be computed by circuits with t gates and compare this number with the total number 2^{2^n} of all Boolean functions.
- The number $F(n, t)$ of circuits of size $\leq t$ with n input variables does not exceed

$$(16(t + n + 2)^2)^t .$$

Each of t gates is assigned one of 16 possible binary Boolean functions that acts on two previous nodes, and each previous node can be either a previous gate ($\leq t$ choices) or a variables or a constant ($\leq n + 2$ choices).

- For $t = 2^n/(10n)$, $F(n, t)$ is approximately $2^{2^n/5}$, which is $\ll 2^{2^n}$.

Random Functions are Complex

- Shannon counting argument: count how many different Boolean functions in n variables can be computed by circuits with t gates and compare this number with the total number 2^{2^n} of all Boolean functions.
- The number $F(n, t)$ of circuits of size $\leq t$ with n input variables does not exceed

$$(16(t + n + 2)^2)^t .$$

Each of t gates is assigned one of 16 possible binary Boolean functions that acts on two previous nodes, and each previous node can be either a previous gate ($\leq t$ choices) or a variables or a constant ($\leq n + 2$ choices).

- For $t = 2^n/(10n)$, $F(n, t)$ is approximately $2^{2^n/5}$, which is $\ll 2^{2^n}$.
- Thus, the circuit complexity of almost all Boolean functions on n variables is exponential in n . Still, we do not know any explicit function with super-linear circuit complexity.

Known Lower Bounds

| | circuit size | formula size |
|--|---|------------------------------|
| full binary basis B_2 | $3n - o(n)$ [Blum] | $n^{2-o(1)}$ [Nechiporuk] |
| basis $U_2 = B_2 \setminus \{\oplus, \equiv\}$ | $5n - o(n)$ [Iwama et al.] | $n^{3-o(1)}$ [Hastad] |
| monotone basis $M_2 = \{\vee, \wedge\}$ | exponential [Razborov; Alon, Boppana; Andreev; Karchmer, Wigderson] | |

Explicit Functions

Explicit Functions

- We are interested in **explicitly defined** Boolean functions of high circuit complexity.

Explicit Functions

- We are interested in **explicitly defined** Boolean functions of high circuit complexity.
- Not explicitly defined function of high circuit complexity: enumerate all Boolean functions on n variables and take the first with circuit complexity at least $2^n/(10n)$.

Explicit Functions

- We are interested in **explicitly defined** Boolean functions of high circuit complexity.
- Not explicitly defined function of high circuit complexity: enumerate all Boolean functions on n variables and take the first with circuit complexity at least $2^n/(10n)$.
- To avoid tricks like this one, we say that a function f is explicitly defined if $f^{-1}(1)$ is in NP.

Explicit Functions

- We are interested in **explicitly defined** Boolean functions of high circuit complexity.
- Not explicitly defined function of high circuit complexity: enumerate all Boolean functions on n variables and take the first with circuit complexity at least $2^n/(10n)$.
- To avoid tricks like this one, we say that a function f is explicitly defined if $f^{-1}(1)$ is in NP.
- Usually, under a Boolean function f we actually understand an infinite sequence $\{f_n \mid n = 1, 2, \dots\}$.

Known Lower Bounds for Circuits over B_2

Known Lower Bounds

$2n - c$ [Schnorr, 74]

$2.5n - o(n)$ [Paul, 77]

$2.5n - c$ [Stockmeyer, 77]

$3n - o(n)$ [Blum, 84]

Known Lower Bounds for Circuits over B_2

Known Lower Bounds

| | |
|---------------|------------------|
| $2n - c$ | [Schnorr, 74] |
| $2.5n - o(n)$ | [Paul, 77] |
| $2.5n - c$ | [Stockmeyer, 77] |
| $3n - o(n)$ | [Blum, 84] |

This Talk

In this talk, we will present a proof of a $7n/3 - c$ lower bound which is as simple as Schnorr's proof of $2n - c$ lower bound.

Known Lower Bounds for Circuits over B_2

Known Lower Bounds

| | |
|---------------|------------------|
| $2n - c$ | [Schnorr, 74] |
| $2.5n - o(n)$ | [Paul, 77] |
| $2.5n - c$ | [Stockmeyer, 77] |
| $3n - o(n)$ | [Blum, 84] |

This Talk

In this talk, we will present a proof of a $7n/3 - c$ lower bound which is as simple as Schnorr's proof of $2n - c$ lower bound.

Gate Elimination

All the proofs are based on the so-called **gate elimination method**. This is essentially the only known method for proving lower bounds on circuit complexity.

Gate Elimination Method

The main idea

Gate Elimination Method

The main idea

- Take an optimal circuit for the function in question.

Gate Elimination Method

The main idea

- Take an optimal circuit for the function in question.
- Setting some variables to constants obtain a subfunction of the same type (in order to proceed by induction) and eliminate several gates.

Gate Elimination Method

The main idea

- Take an optimal circuit for the function in question.
- Setting some variables to constants obtain a subfunction of the same type (in order to proceed by induction) and eliminate several gates.
- A gate is eliminated if it computes a constant or a variable.

Gate Elimination Method

The main idea

- Take an optimal circuit for the function in question.
- Setting some variables to constants obtain a subfunction of the same type (in order to proceed by induction) and eliminate several gates.
- A gate is eliminated if it computes a constant or a variable.
- By repeatedly applying this process, conclude that the original circuit must have had many gates.

Gate Elimination Method


The main idea

- Take an optimal circuit for the function in question.
- Setting some variables to constants obtain a subfunction of the same type (in order to proceed by induction) and eliminate several gates.
- A gate is eliminated if it computes a constant or a variable.
- By repeatedly applying this process, conclude that the original circuit must have had many gates.


Remark

This method is very unlikely to produce non-linear lower bounds.


Example

 

Example

 


Example

 


G_5 now computes $G_3 \oplus 1 = \neg G_3$

Example

 


Example

 


now we can change the binary function assigned to G_6

Example

 


Example

 


now assign $x_3 = 0$

Example

 


G_1 then is equal to x_2

Example

 


Example

 

$$G_2 = x_4$$

Example

 

The Class $Q_{2,3}^n$

Definition

A function $f: \{0, 1\}^n \rightarrow \{0, 1\}$ belongs to the class $Q_{2,3}^n$ if

The Class $Q_{2,3}^n$

Definition

A function $f: \{0, 1\}^n \rightarrow \{0, 1\}$ belongs to the class $Q_{2,3}^n$ if

- 1 for all different $i, j \in \{1, \dots, n\}$, one obtains at least three different subfunctions by replacing x_i and x_j by constants;

The Class $Q_{2,3}^n$

Definition

A function $f: \{0, 1\}^n \rightarrow \{0, 1\}$ belongs to the class $Q_{2,3}^n$ if

- 1 for all different $i, j \in \{1, \dots, n\}$, one obtains at least three different subfunctions by replacing x_i and x_j by constants;
- 2 for all $i \in \{1, \dots, n\}$, one obtains a subfunction in $Q_{2,3}^{n-1}$ (if $n \geq 4$) by replacing x_i by any constant.

The Class $Q_{2,3}^n$

Definition

A function $f: \{0, 1\}^n \rightarrow \{0, 1\}$ belongs to the class $Q_{2,3}^n$ if

- 1 for all different $i, j \in \{1, \dots, n\}$, one obtains at least three different subfunctions by replacing x_i and x_j by constants;
- 2 for all $i \in \{1, \dots, n\}$, one obtains a subfunction in $Q_{2,3}^{n-1}$ (if $n \geq 4$) by replacing x_i by any constant.

Modular functions

The Class $Q_{2,3}^n$

Definition

A function $f: \{0, 1\}^n \rightarrow \{0, 1\}$ belongs to the class $Q_{2,3}^n$ if

- 1 for all different $i, j \in \{1, \dots, n\}$, one obtains at least three different subfunctions by replacing x_i and x_j by constants;
- 2 for all $i \in \{1, \dots, n\}$, one obtains a subfunction in $Q_{2,3}^{n-1}$ (if $n \geq 4$) by replacing x_i by any constant.

Modular functions

- Let $\text{MOD}_{m,r}^n(x_1, \dots, x_n) = 1$ iff $\sum_{i=1}^n x_i \equiv r \pmod{m}$.

The Class $Q_{2,3}^n$

Definition

A function $f: \{0, 1\}^n \rightarrow \{0, 1\}$ belongs to the class $Q_{2,3}^n$ if

- 1 for all different $i, j \in \{1, \dots, n\}$, one obtains at least three different subfunctions by replacing x_i and x_j by constants;
- 2 for all $i \in \{1, \dots, n\}$, one obtains a subfunction in $Q_{2,3}^{n-1}$ (if $n \geq 4$) by replacing x_i by any constant.

Modular functions

- Let $\text{MOD}_{m,r}^n(x_1, \dots, x_n) = 1$ iff $\sum_{i=1}^n x_i \equiv r \pmod{m}$.
- Then $\text{MOD}_{3,r}^n, \text{MOD}_{4,r}^n \in Q_{2,3}^n$, but $\text{MOD}_{2,r}^n \notin Q_{2,3}^n$.

Schnorr's $2n$ Lower Bound

Theorem

If $f \in Q_{2,3}^n$, then $C(f) \geq 2n - 8$.

Schnorr's $2n$ Lower Bound

Theorem

If $f \in Q_{2,3}^n$, then $C(f) \geq 2n - 8$.

Proof

Schnorr's $2n$ Lower Bound

Theorem

If $f \in Q_{2,3}^n$, then $C(f) \geq 2n - 8$.

Proof

- Induction on n . If $n \leq 4$, then the statement is trivial.

Schnorr's $2n$ Lower Bound

Theorem

If $f \in Q_{2,3}^n$, then $C(f) \geq 2n - 8$.

Proof

- Induction on n . If $n \leq 4$, then the statement is trivial.
- Consider an optimal circuit and its top gate Q which is fed by different variables x_i and x_j (they are different, since the circuit is optimal).

Schnorr's $2n$ Lower Bound

Theorem

If $f \in Q_{2,3}^n$, then $C(f) \geq 2n - 8$.

Proof

- Induction on n . If $n \leq 4$, then the statement is trivial.
- Consider an optimal circuit and its top gate Q which is fed by different variables x_i and x_j (they are different, since the circuit is optimal).
- Note that $Q = Q(x_i, x_j)$ can only take **two** values, 0 and 1, when x_i and x_j are fixed.

Schnorr's $2n$ Lower Bound

Theorem

If $f \in Q_{2,3}^n$, then $C(f) \geq 2n - 8$.

Proof

- Induction on n . If $n \leq 4$, then the statement is trivial.
- Consider an optimal circuit and its top gate Q which is fed by different variables x_i and x_j (they are different, since the circuit is optimal).
- Note that $Q = Q(x_i, x_j)$ can only take **two** values, 0 and 1, when x_i and x_j are fixed.
- Thus, either x_i or x_j fans out to another gate P .

Schnorr's $2n$ Lower Bound

Theorem

If $f \in Q_{2,3}^n$, then $C(f) \geq 2n - 8$.

Proof

- Induction on n . If $n \leq 4$, then the statement is trivial.
- Consider an optimal circuit and its top gate Q which is fed by different variables x_i and x_j (they are different, since the circuit is optimal).
- Note that $Q = Q(x_i, x_j)$ can only take **two** values, 0 and 1, when x_i and x_j are fixed.
- Thus, either x_i or x_j fans out to another gate P .
- By assigning this variable, we eliminate at least two gates and get a subfunction from $Q_{2,3}^{n-1}$. □

AND-type Gates vs XOR-type Gates

Binary functions

The set B_2 of all binary functions contains 16 functions $f(x, y)$:

AND-type Gates vs XOR-type Gates

Binary functions

The set B_2 of all binary functions contains 16 functions $f(x, y)$:

- 1 2 constants: 0, 1

AND-type Gates vs XOR-type Gates

Binary functions

The set B_2 of all binary functions contains 16 functions $f(x, y)$:

- 1 2 constants: 0, 1
- 2 4 degenerate functions: x , \bar{x} , y , \bar{y} .

AND-type Gates vs XOR-type Gates

Binary functions

The set B_2 of all binary functions contains 16 functions $f(x, y)$:

- 1 2 constants: 0, 1
- 2 4 degenerate functions: x, \bar{x}, y, \bar{y} .
- 3 2 XOR-type functions: $x \oplus y \oplus a$, where $a \in \{0, 1\}$.

AND-type Gates vs XOR-type Gates

Binary functions

The set B_2 of all binary functions contains 16 functions $f(x, y)$:

- 1 2 constants: $0, 1$
- 2 4 degenerate functions: x, \bar{x}, y, \bar{y} .
- 3 2 XOR-type functions: $x \oplus y \oplus a$, where $a \in \{0, 1\}$.
- 4 8 AND-type functions: $(x \oplus a)(y \oplus b) \oplus c$, where $a, b, c \in \{0, 1\}$.

AND-type Gates vs XOR-type Gates

Binary functions

The set B_2 of all binary functions contains 16 functions $f(x, y)$:

- 1 2 constants: $0, 1$
- 2 4 degenerate functions: x, \bar{x}, y, \bar{y} .
- 3 2 XOR-type functions: $x \oplus y \oplus a$, where $a \in \{0, 1\}$.
- 4 8 AND-type functions: $(x \oplus a)(y \oplus b) \oplus c$, where $a, b, c \in \{0, 1\}$.

Remark

Optimal circuits contain AND- and XOR-type gates **only**, as constant and degenerate gates can be easily eliminated.

AND-type Gates vs XOR-type Gates

AND-type Gates vs XOR-type Gates

AND-type Gates vs XOR-type Gates

AND-type Gates vs XOR-type Gates

- AND-type gates are easier to handle than XOR-type gates.

AND-type Gates vs XOR-type Gates

AND-type Gates vs XOR-type Gates

- AND-type gates are easier to handle than XOR-type gates.
- Let $Q(x_i, x_j) = (x_i \oplus a)(x_j \oplus b) \oplus c$ be an AND-type gate. Then by assigning $x_i = a$ or $x_j = b$ we make this gate constant. That is, **we eliminate not only this gate, but also all its direct successors!**

AND-type Gates vs XOR-type Gates

AND-type Gates vs XOR-type Gates

- AND-type gates are easier to handle than XOR-type gates.
- Let $Q(x_i, x_j) = (x_i \oplus a)(x_j \oplus b) \oplus c$ be an AND-type gate. Then by assigning $x_i = a$ or $x_j = b$ we make this gate constant. That is, **we eliminate not only this gate, but also all its direct successors!**
- While by assigning any constant to x_i , we obtain from $Q(x_i, x_j) = x_i \oplus x_j \oplus c$ either x_j or \bar{x}_j .

AND-type Gates vs XOR-type Gates

AND-type Gates vs XOR-type Gates

- AND-type gates are easier to handle than XOR-type gates.
- Let $Q(x_i, x_j) = (x_i \oplus a)(x_j \oplus b) \oplus c$ be an AND-type gate. Then by assigning $x_i = a$ or $x_j = b$ we make this gate constant. That is, **we eliminate not only this gate, but also all its direct successors!**
- While by assigning any constant to x_i , we obtain from $Q(x_i, x_j) = x_i \oplus x_j \oplus c$ either x_j or \bar{x}_j .
- That is why, in particular, the current record bounds for circuits over $U_2 = B_2 \setminus \{\oplus, \equiv\}$ are stronger than the bounds over B_2 .

AND-type Gates vs XOR-type Gates

AND-type Gates vs XOR-type Gates

- AND-type gates are easier to handle than XOR-type gates.
- Let $Q(x_i, x_j) = (x_i \oplus a)(x_j \oplus b) \oplus c$ be an AND-type gate. Then by assigning $x_i = a$ or $x_j = b$ we make this gate constant. That is, **we eliminate not only this gate, but also all its direct successors!**
- While by assigning any constant to x_i , we obtain from $Q(x_i, x_j) = x_i \oplus x_j \oplus c$ either x_j or \bar{x}_j .
- That is why, in particular, the current record bounds for circuits over $U_2 = B_2 \setminus \{\oplus, \equiv\}$ are stronger than the bounds over B_2 .
- Usually, the main bottleneck of a proof based on gate elimination is a circuit whose top contains many XOR-type gates.

Polynomials over $\text{GF}(2)$

Polynomials over $\text{GF}(2)$

Polynomials over $\text{GF}(2)$

Polynomials over $\text{GF}(2)$

- Let $\tau(f)$ denote the unique polynomial over $\text{GF}(2)$ representing f .

Polynomials over $\text{GF}(2)$

Polynomials over $\text{GF}(2)$

- Let $\tau(f)$ denote the unique polynomial over $\text{GF}(2)$ representing f .
- E.g., $\tau(\text{MOD}_{3,0}^3) = x_1x_2x_3 + (1 - x_1)(1 - x_2)(1 - x_3)$.

Polynomials over $\text{GF}(2)$

Polynomials over $\text{GF}(2)$

- Let $\tau(f)$ denote the unique polynomial over $\text{GF}(2)$ representing f .
- E.g., $\tau(\text{MOD}_{3,0}^3) = x_1x_2x_3 + (1 - x_1)(1 - x_2)(1 - x_3)$.
- Note that $\tau(f)$ is multi-linear.

Polynomials over $\text{GF}(2)$

Polynomials over $\text{GF}(2)$

- Let $\tau(f)$ denote the unique polynomial over $\text{GF}(2)$ representing f .
- E.g., $\tau(\text{MOD}_{3,0}^3) = x_1x_2x_3 + (1 - x_1)(1 - x_2)(1 - x_3)$.
- Note that $\tau(f)$ is multi-linear.
- It can be easily shown that, for any r , $\deg(\tau(\text{MOD}_{4,r}^n)) \leq 3$, while $\deg(\tau(\text{MOD}_{3,r}^n)) \geq n - 1$.

Polynomials over $\text{GF}(2)$

Polynomials over $\text{GF}(2)$

- Let $\tau(f)$ denote the unique polynomial over $\text{GF}(2)$ representing f .
- E.g., $\tau(\text{MOD}_{3,0}^3) = x_1x_2x_3 + (1 - x_1)(1 - x_2)(1 - x_3)$.
- Note that $\tau(f)$ is multi-linear.
- It can be easily shown that, for any r , $\deg(\tau(\text{MOD}_{4,r}^n)) \leq 3$, while $\deg(\tau(\text{MOD}_{3,r}^n)) \geq n - 1$.

Lemma (Degree lower bound)

Any circuit computing f contains at least $\deg(\tau(f)) - 1$ AND-type gates.

Combined Complexity Measure

Idea

Thus, in a bottleneck case we see only XOR-type gates, however we are given several AND-type gates in advance.

Combined Complexity Measure

Idea

Thus, in a bottleneck case we see only XOR-type gates, however we are given several AND-type gates in advance. Let us increase the weight of a XOR-type gate.

Combined Complexity Measure

Idea

Thus, in a bottleneck case we see only XOR-type gates, however we are given several AND-type gates in advance. Let us increase the weight of a XOR-type gate.

Definition

For a circuit C , let $A(C)$ and $X(C)$ denote the number of AND- and XOR-type gates in C , respectively. Let also $\mu(C) = 3X(C) + 2A(C)$.

An Improved Lower Bound

Lemma

For any circuit C computing $f \in Q_{2,3}^n$, $\mu(C) = 3X(C) + 2A(C) \geq 6n - 24$.

An Improved Lower Bound

Lemma

For any circuit C computing $f \in Q_{2,3}^n$, $\mu(C) = 3X(C) + 2A(C) \geq 6n - 24$.

Proof

An Improved Lower Bound

Lemma

For any circuit C computing $f \in Q_{2,3}^n$, $\mu(C) = 3X(C) + 2A(C) \geq 6n - 24$.

Proof

- As in the previous proof, we consider a top gate $Q(x_i, x_j)$ and assume wlog that x_i feeds also another gate P .



An Improved Lower Bound

Lemma

For any circuit C computing $f \in Q_{2,3}^n$, $\mu(C) = 3X(C) + 2A(C) \geq 6n - 24$.

Proof

  - As in the previous proof, we consider a top gate $Q(x_i, x_j)$ and assume wlog that x_i feeds also another gate P .
- There are two cases:





An Improved Lower Bound

Lemma

For any circuit C computing $f \in Q_{2,3}^n$, $\mu(C) = 3X(C) + 2A(C) \geq 6n - 24$.

Proof

  - As in the previous proof, we consider a top gate $Q(x_i, x_j)$ and assume wlog that x_i feeds also another gate P .
- There are two cases:



- In both cases, we can assign x_i a constant such that μ is reduced at least by 6. □

$7n/3$ Lower Bound

Lemma

Let $f \in Q_{2,3}^n$ and $\deg(\tau(f)) \geq n - c$, then $C(f) \geq 7n/3 - c'$.

$7n/3$ Lower Bound

Lemma

Let $f \in Q_{2,3}^n$ and $\deg(\tau(f)) \geq n - c$, then $C(f) \geq 7n/3 - c'$.

proof

Let C be an optimal circuit computing f .

$7n/3$ Lower Bound

Lemma

Let $f \in Q_{2,3}^n$ and $\deg(\tau(f)) \geq n - c$, then $C(f) \geq 7n/3 - c'$.

proof

Let C be an optimal circuit computing f .

$$\begin{array}{r} 3X(C) + 2A(C) \geq 6n - 24 \\ A(C) \geq n - c - 1 \\ \hline C(f) = 3X(C) + 3A(C) \geq 7n - 25 - c \end{array}$$



Further Improvements

Further Improvements

- Prove a stronger lower bound on μ . A more involved case analysis is needed.

Further Improvements

- Prove a stronger lower bound on μ . A more involved case analysis is needed.
- Prove stronger lower bound on $A(C)$.

Further Improvements

- Prove a stronger lower bound on μ . A more involved case analysis is needed.
- Prove stronger lower bound on $A(C)$.
 - Remind that $\tau(\text{MOD}_3^n) = x_1 x_2 \dots x_n + \dots$, so any circuit computing MOD_3^n must have at least $(n - 1)$ AND-type gates just in order to compute this monomial.

Further Improvements

- Prove a stronger lower bound on μ . A more involved case analysis is needed.
- Prove stronger lower bound on $A(C)$.
 - Remind that $\tau(\text{MOD}_3^n) = x_1x_2 \dots x_n + \dots$, so any circuit computing MOD_3^n must have at least $(n - 1)$ AND-type gates just in order to compute this monomial.
 - Probably, more AND-type gates are needed to compute all the other monomials?

Further Improvements

- Prove a stronger lower bound on μ . A more involved case analysis is needed.
- Prove stronger lower bound on $A(C)$.
 - Remind that $\tau(\text{MOD}_3^n) = x_1 x_2 \dots x_n + \dots$, so any circuit computing MOD_3^n must have at least $(n - 1)$ AND-type gates just in order to compute this monomial.
 - Probably, more AND-type gates are needed to compute all the other monomials?
 - No, there is a circuit computing MOD_3^n of size $3n$ containing exactly n AND-type gates.

Further Improvements

- Prove a stronger lower bound on μ . A more involved case analysis is needed.
- Prove stronger lower bound on $A(C)$.
 - Remind that $\tau(\text{MOD}_3^n) = x_1x_2 \dots x_n + \dots$, so any circuit computing MOD_3^n must have at least $(n - 1)$ AND-type gates just in order to compute this monomial.
 - Probably, more AND-type gates are needed to compute all the other monomials?
 - No, there is a circuit computing MOD_3^n of size $3n$ containing exactly n AND-type gates.
 - Moreover, any symmetric function can be computed using only n AND-type gates.

Further Improvements

- Prove a stronger lower bound on μ . A more involved case analysis is needed.
- Prove stronger lower bound on $A(C)$.
 - Remind that $\tau(\text{MOD}_3^n) = x_1x_2 \dots x_n + \dots$, so any circuit computing MOD_3^n must have at least $(n - 1)$ AND-type gates just in order to compute this monomial.
 - Probably, more AND-type gates are needed to compute all the other monomials?
 - No, there is a circuit computing MOD_3^n of size $3n$ containing exactly n AND-type gates.
 - Moreover, any symmetric function can be computed using only n AND-type gates.
 - No lower bound better than $n - 1$ is known! Though the multiplicative complexity of almost all functions is exponential.

MOD₃ vs MOD₄

MOD₃ is not simpler than MOD₄

For circuits and formulas over B_2 and U_2 , it is known that MOD₃ is not simpler than MOD₄. The exact complexity of MOD₄ is known for some of these models: $C_{B_2}(\text{MOD}_4^n) = 2.5n - c$, $L_{B_2}(\text{MOD}_4^n) = \Theta(n \log n)$. The exact complexity of MOD₃ is known for none of these models.

MOD₃ vs MOD₄

MOD₃ is not simpler than MOD₄

For circuits and formulas over B_2 and U_2 , it is known that MOD₃ is not simpler than MOD₄. The exact complexity of MOD₄ is known for some of these models: $C_{B_2}(\text{MOD}_4^n) = 2.5n - c$, $L_{B_2}(\text{MOD}_4^n) = \Theta(n \log n)$. The exact complexity of MOD₃ is known for none of these models.

Why MOD₃ must be harder than MOD₄?

MOD₃ vs MOD₄

MOD₃ is not simpler than MOD₄

For circuits and formulas over B_2 and U_2 , it is known that MOD₃ is not simpler than MOD₄. The exact complexity of MOD₄ is known for some of these models: $C_{B_2}(\text{MOD}_4^n) = 2.5n - c$, $L_{B_2}(\text{MOD}_4^n) = \Theta(n \log n)$. The exact complexity of MOD₃ is known for none of these models.

Why MOD₃ must be harder than MOD₄?

- 4 is a power of 2, 3 is not. To compute MOD₄ⁿ, compute the bit representation of $\sum x_i$ and check the last two bits.

MOD₃ vs MOD₄

MOD₃ is not simpler than MOD₄

For circuits and formulas over B_2 and U_2 , it is known that MOD₃ is not simpler than MOD₄. The exact complexity of MOD₄ is known for some of these models: $C_{B_2}(\text{MOD}_4^n) = 2.5n - c$, $L_{B_2}(\text{MOD}_4^n) = \Theta(n \log n)$. The exact complexity of MOD₃ is known for none of these models.

Why MOD₃ must be harder than MOD₄?

- 4 is a power of 2, 3 is not. To compute MOD₄ⁿ, compute the bit representation of $\sum x_i$ and check the last two bits.
- MOD₃ survives under substitutions like $x_i = x_j$.

MOD₃ vs MOD₄

MOD₃ is not simpler than MOD₄

For circuits and formulas over B_2 and U_2 , it is known that MOD₃ is not simpler than MOD₄. The exact complexity of MOD₄ is known for some of these models: $C_{B_2}(\text{MOD}_4^n) = 2.5n - c$, $L_{B_2}(\text{MOD}_4^n) = \Theta(n \log n)$. The exact complexity of MOD₃ is known for none of these models.

Why MOD₃ must be harder than MOD₄?

- 4 is a power of 2, 3 is not. To compute MOD₄ⁿ, compute the bit representation of $\sum x_i$ and check the last two bits.
- MOD₃ survives under substitutions like $x_i = x_j$.
- $C_{B_2}(\text{MOD}_3^n)$ for $n \leq 5$ “grows like” $3n$.

Open Problems

- 1 Close the gaps:

$$2.5n \leq C_{B_2}(\text{MOD}_3^n) \leq 3n$$

$$4n \leq C_{U_2}(\text{MOD}_4^n) \leq 5n$$

Open Problems

- 1 Close the gaps:

$$2.5n \leq C_{B_2}(\text{MOD}_3^n) \leq 3n$$

$$4n \leq C_{U_2}(\text{MOD}_4^n) \leq 5n$$

- 2 Prove a cn lower bound (for a constant $c > 1$) on the multiplicative complexity of an explicit Boolean function.

Thank you for your attention!