

An Elementary Proof of a $3n - o(n)$ Lower Bound on Circuit Complexity of Affine Dispersers

E. Demenkov and A. Kulikov

Steklov Institute of Mathematics at St. Petersburg

Estonian Theory Days
08 October 2011

Boolean Circuits

Inputs:

$x_1, x_2, \dots, x_n, 0, 1$

Gates:

binary functions

Fan-out:

unbounded


$$g_1 = x_1 \oplus x_2$$

$$g_2 = x_2 \wedge x_3$$

$$g_3 = g_1 \vee g_2$$

$$g_4 = g_2 \vee 1$$

$$g_5 = g_3 \equiv g_4$$

 

Random Functions are Complex

- Shannon counting argument: count how many different Boolean functions in n variables can be computed by circuits with t gates and compare this number with the total number 2^{2^n} of all Boolean functions.

Random Functions are Complex

- Shannon counting argument: count how many different Boolean functions in n variables can be computed by circuits with t gates and compare this number with the total number 2^{2^n} of all Boolean functions.
- The number $F(n, t)$ of circuits of size $\leq t$ with n input variables does not exceed

$$(16(t + n + 2)^2)^t .$$

Each of t gates is assigned one of 16 possible binary Boolean functions that acts on two previous nodes, and each previous node can be either a previous gate ($\leq t$ choices) or a variables or a constant ($\leq n + 2$ choices).

Random Functions are Complex

- Shannon counting argument: count how many different Boolean functions in n variables can be computed by circuits with t gates and compare this number with the total number 2^{2^n} of all Boolean functions.
- The number $F(n, t)$ of circuits of size $\leq t$ with n input variables does not exceed

$$(16(t + n + 2)^2)^t.$$

Each of t gates is assigned one of 16 possible binary Boolean functions that acts on two previous nodes, and each previous node can be either a previous gate ($\leq t$ choices) or a variables or a constant ($\leq n + 2$ choices).

- For $t = 2^n/(10n)$, $F(n, t)$ is approximately $2^{2^n/5}$, which is $\ll 2^{2^n}$.

Random Functions are Complex

- Shannon counting argument: count how many different Boolean functions in n variables can be computed by circuits with t gates and compare this number with the total number 2^{2^n} of all Boolean functions.
- The number $F(n, t)$ of circuits of size $\leq t$ with n input variables does not exceed

$$(16(t + n + 2)^2)^t.$$

Each of t gates is assigned one of 16 possible binary Boolean functions that acts on two previous nodes, and each previous node can be either a previous gate ($\leq t$ choices) or a variables or a constant ($\leq n + 2$ choices).

- For $t = 2^n/(10n)$, $F(n, t)$ is approximately $2^{2^n/5}$, which is $\ll 2^{2^n}$.
- Thus, the circuit complexity of almost all Boolean functions on n variables is exponential in n . Still, we do not know any explicit function with super-linear circuit complexity.

Known Lower Bounds

	circuit size	formula size
full binary basis B_2	$3n - o(n)$ [Blum]	$n^{2-o(1)}$ [Nechiporuk]
basis $U_2 = B_2 \setminus \{\oplus, \equiv\}$	$5n - o(n)$ [Iwama et al.]	$n^{3-o(1)}$ [Hastad]
monotone basis $M_2 = \{\vee, \wedge\}$	exponential [Razborov; Alon, Boppana; Andreev; Karchmer, Wigderson]	

Known Lower Bounds for Circuits over B_2

Known Lower Bounds

$2n - c$ [Kloss and Malyshev, 65]

$2n - c$ [Schnorr, 74]

$2.5n - o(n)$ [Paul, 77]

$2.5n - c$ [Stockmeyer, 77]

$3n - o(n)$ [Blum, 84]

Known Lower Bounds for Circuits over B_2

Known Lower Bounds

$2n - c$	[Kloss and Malyshev, 65]
$2n - c$	[Schnorr, 74]
$2.5n - o(n)$	[Paul, 77]
$2.5n - c$	[Stockmeyer, 77]
$3n - o(n)$	[Blum, 84]

This Talk

In this talk, we will present a new proof of a $3n - o(n)$ lower. The proof is much simpler than Blum's proof, however the function used is much more complicated.

Gate Elimination Method

Gate Elimination

All the proofs are based on the so-called **gate elimination method**. This is essentially the only known method for proving lower bounds on circuit complexity.

Gate Elimination Method

Gate Elimination

All the proofs are based on the so-called **gate elimination method**. This is essentially the only known method for proving lower bounds on circuit complexity.

The main idea

- Take an optimal circuit for the function in question.

Gate Elimination Method

Gate Elimination

All the proofs are based on the so-called **gate elimination method**. This is essentially the only known method for proving lower bounds on circuit complexity.

The main idea

- Take an optimal circuit for the function in question.
- Setting some variables to constants obtain a subfunction of the same type (in order to proceed by induction) and eliminate several gates.

Gate Elimination Method

Gate Elimination

All the proofs are based on the so-called **gate elimination method**. This is essentially the only known method for proving lower bounds on circuit complexity.

The main idea

- Take an optimal circuit for the function in question.
- Setting some variables to constants obtain a subfunction of the same type (in order to proceed by induction) and eliminate several gates.
- A gate is eliminated if it computes a constant or a variable.

Gate Elimination Method

Gate Elimination

All the proofs are based on the so-called **gate elimination method**. This is essentially the only known method for proving lower bounds on circuit complexity.

The main idea

- Take an optimal circuit for the function in question.
- Setting some variables to constants obtain a subfunction of the same type (in order to proceed by induction) and eliminate several gates.
- A gate is eliminated if it computes a constant or a variable.
- By repeatedly applying this process, conclude that the original circuit must have had many gates.

Gate Elimination Method

Gate Elimination

All the proofs are based on the so-called **gate elimination method**. This is essentially the only known method for proving lower bounds on circuit complexity.

The main idea

- Take an optimal circuit for the function in question.
- Setting some variables to constants obtain a subfunction of the same type (in order to proceed by induction) and eliminate several gates.
- A gate is eliminated if it computes a constant or a variable.
- By repeatedly applying this process, conclude that the original circuit must have had many gates.

Gate Elimination Method

Gate Elimination

All the proofs are based on the so-called **gate elimination method**. This is essentially the only known method for proving lower bounds on circuit complexity.


The main idea

- Take an optimal circuit for the function in question.
- Setting some variables to constants obtain a subfunction of the same type (in order to proceed by induction) and eliminate several gates.
- A gate is eliminated if it computes a constant or a variable.
- By repeatedly applying this process, conclude that the original circuit must have had many gates.


Remark

This method is very unlikely to produce non-linear lower bounds.


Example

 

Example

 


Example

 


G_5 now computes $G_3 \oplus 1 = \neg G_3$

Example

 


Example

 


now we can change the binary function assigned to G_6

Example

 


Example

 


now assign $x_3 = 0$

Example

 


G_1 then is equal to x_2


Example

 


Example

 

Example

 


A Typical Bottleneck

 

A Typical Bottleneck

 
this is how a typical bottleneck case looks like



A Typical Bottleneck

this is how a typical bottleneck case looks like

 by assigning a variable we cannot kill more than 2 gates




A Typical Bottleneck

this is how a typical bottleneck case looks like

by assigning a variable we cannot kill more than 2 gates

 at the same time we cannot exclude that a top of a circuit looks like this




A Typical Bottleneck

this is how a typical bottleneck case looks like

by assigning a variable we cannot kill more than 2 gates

at the same time we cannot exclude that a top of a circuit looks like this

 consider a substitution $x_1 \oplus x_2 \oplus x_3 = 0$: under it G_5 trivializes



Affine Dispersers

- OK, linear substitutions do help in gate elimination, but where is a function that survives under such substitutions?

Affine Dispersers

- OK, linear substitutions do help in gate elimination, but where is a function that survives under such substitutions?
- Constructing a function that does not become a constant after any $n - o(n)$ linear substitutions is non-trivial. E.g., any symmetric function may be turned into a constant after $n/2$ linear substitutions:
 $x_1 \oplus x_2 = 1, x_3 \oplus x_4 = 1, \dots$

Affine Dispersers

- OK, linear substitutions do help in gate elimination, but where is a function that survives under such substitutions?
- Constructing a function that does not become a constant after any $n - o(n)$ linear substitutions is non-trivial. E.g., any symmetric function may be turned into a constant after $n/2$ linear substitutions: $x_1 \oplus x_2 = 1, x_3 \oplus x_4 = 1, \dots$
- An object that we are looking for is called an **affine disperser**.


Affine Dispersers

- OK, linear substitutions do help in gate elimination, but where is a function that survives under such substitutions?
- Constructing a function that does not become a constant after any $n - o(n)$ linear substitutions is non-trivial. E.g., any symmetric function may be turned into a constant after $n/2$ linear substitutions: $x_1 \oplus x_2 = 1, x_3 \oplus x_4 = 1, \dots$
- An object that we are looking for is called an **affine disperser**.
- Formally, an affine disperser for dimension d is a function $f: \{0, 1\}^n \rightarrow \{0, 1\}$ that is not constant on any affine subspace of $\{0, 1\}^n$ of dimension at least d .

Affine Dispersers


- OK, linear substitutions do help in gate elimination, but where is a function that survives under such substitutions?
- Constructing a function that does not become a constant after any $n - o(n)$ linear substitutions is non-trivial. E.g., any symmetric function may be turned into a constant after $n/2$ linear substitutions: $x_1 \oplus x_2 = 1, x_3 \oplus x_4 = 1, \dots$
- An object that we are looking for is called an **affine disperser**.
- Formally, an affine disperser for dimension d is a function $f: \{0, 1\}^n \rightarrow \{0, 1\}$ that is not constant on any affine subspace of $\{0, 1\}^n$ of dimension at least d .
- Only recently, an explicit affine disperser for $d = o(n)$ was constructed [Ben-Sasson and Kopparty, 09].

Proof Idea

 


Proof Idea

 take the first gate which is not a
XOR of out-degree 1



Proof Idea

 
take the first gate which is not a
XOR of out-degree 1



Proof Idea

take the first gate which is not a
XOR of out-degree 1


both its inputs compute linear
functions

 

Proof Idea

take the first gate which is not a XOR of out-degree 1

both its inputs compute linear functions

 


Proof Idea

take the first gate which is not a XOR of out-degree 1

both its inputs compute linear functions

make a substitution
 
$$x_1 \oplus x_2 \oplus x_3 \oplus x_5 \oplus x_6 = 1$$



Proof Idea


take the first gate which is not a XOR of out-degree 1

both its inputs compute linear functions

make a substitution

$$x_1 \oplus x_2 \oplus x_3 \oplus x_5 \oplus x_6 = 1$$

 this kills the considered gate and all its successors



Proof Idea


take the first gate which is not a XOR of out-degree 1

both its inputs compute linear functions

make a substitution

$$x_1 \oplus x_2 \oplus x_3 \oplus x_5 \oplus x_6 = 1$$

 this kills the considered gate and all its successors



Proof Idea

take the first gate which is not a XOR of out-degree 1


both its inputs compute linear functions

make a substitution

$$x_1 \oplus x_2 \oplus x_3 \oplus x_5 \oplus x_6 = 1$$

this kills the considered gate and all its successors

 moreover, all its predecessors are not needed any more



Proof Idea

take the first gate which is not a XOR of out-degree 1


both its inputs compute linear functions

make a substitution

$$x_1 \oplus x_2 \oplus x_3 \oplus x_5 \oplus x_6 = 1$$


this kills the considered gate and all its successors

 moreover, all its predecessors are not needed any more



Proof Idea

 by a short case analysis it is possible to show that this way one can always eliminate 3 gates; since we can make $n - o(n)$ such substitutions a lower bound $3n - o(n)$ follows



Thank you for your attention!